

① 
$$V_c(t) = \frac{1}{C} \int_0^t i_c(t) dt ;$$

$$T = \frac{1}{f} = 2 \text{ ms}; \quad \frac{T}{2} = 1 \text{ ms}; \quad \int_0^{T/2} i_c(t) dt = \frac{I_m \cdot T}{2} = \frac{5 \cdot 10^{-3}}{2} = 2,5 \text{ mC}$$

a)  $t_1 = \frac{T}{2} = 1 \text{ ms}; \quad V_c(t_1) = \frac{1}{C} \int_0^{t_1} i_c(t) dt = \frac{2,5 \cdot 10^{-3}}{12 \cdot 10^{-6}} = 208,3 \text{ V}$

b)  $t_2 = T = 2 \text{ ms}; \quad W_1 = \frac{1}{2} \cdot 12 \cdot 10^{-6} \cdot 208,3^2 = 0,26 \text{ J}$

$$V_c(t_2) = \frac{1}{C} \int_0^{t_1} i_c(t) dt + \frac{1}{C} \int_{t_1}^{t_2} i_c(t) dt$$

$$V_c(t_2) = \frac{2,5 \cdot 10^{-3}}{12 \cdot 10^{-6}} - \frac{2,5 \cdot 10^{-3}}{12 \cdot 10^{-6}} = 0 ; \quad W_2 = 0$$

c)  $t_3 = \frac{3T}{2} = 3 \text{ ms};$

$$V_c(t_3) = \frac{1}{C} \int_0^{t_1} i_c(t) dt + \frac{1}{C} \int_{t_1}^{t_2} i_c(t) dt + \frac{1}{C} \int_{t_2}^{t_3} i_c(t) dt$$

$$V_c(t_3) = \frac{2,5 \cdot 10^{-3}}{12 \cdot 10^{-6}} - \frac{2,5 \cdot 10^{-3}}{12 \cdot 10^{-6}} + \frac{2,5 \cdot 10^{-3}}{12 \cdot 10^{-6}} = 208,3 \text{ V}; \quad W_3 = W_1$$

② 
$$V_c(t) = V_c(\infty) + [V_c(0) - V_c(\infty)] e^{-t/\tau};$$

$$V_c(0) = R_2 I_{in1} = 2,2 \cdot 10^3 \cdot 20 \cdot 10^{-3} = 44 \text{ V};$$




$$V_c(\infty) = R_2 I_{in2} = 2,2 \cdot 10^3 \cdot 10 \cdot 10^{-3} = 22 \text{ V}$$

$$\tau = R_2 C = 2,2 \cdot 10^3 \cdot 10^{-6} = 2,2 \text{ ms}$$

$$30 = 22 + [44 - 22] e^{-t_1/\tau}$$

$$8 = 22 \cdot e^{-t_1/\tau}$$
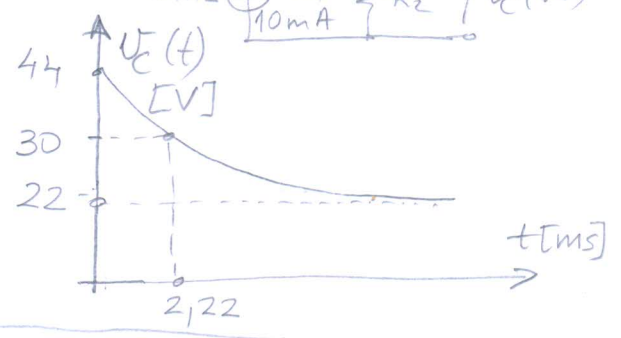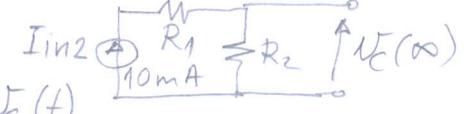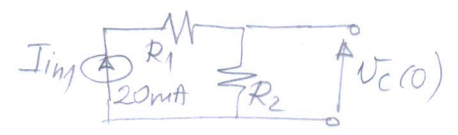
$$t_1 = \tau \cdot \ln \frac{22}{8} = 2,22 \text{ ms}$$



③ 
$$V_o = -V_s \frac{R_x}{R_i} + V_{ref} \left(1 + \frac{R_x}{R_i}\right)$$

$$V_s(0) = 0,6 \text{ V}$$

$$0 = -0,6 \frac{R_x}{R_i} + V_{ref} \left(1 + \frac{R_x}{R_i}\right) > -$$

$$V_s(100) = 0,6 - 100 \cdot 2 \cdot 10^{-3} = 0,4 \text{ V}$$

$$5 = -0,4 \frac{R_x}{R_i} + V_{ref} \left(1 + \frac{R_x}{R_i}\right)$$

$$5 = 0,2 \cdot \frac{R_x}{R_i} \Rightarrow \frac{R_x}{R_i} = 25; \quad R_x = 25 R_i = 250 \text{ k}\Omega$$

$$V_{ref} \left(1 + \frac{R_x}{R_i}\right) = 0,6 \frac{R_x}{R_i}; \quad V_{ref} \cdot 26 = 0,6 \cdot 50$$

$$V_{ref} = \frac{0,6 \cdot 25}{26} = 577 \text{ mV}$$