

$$V_{BB} = \frac{R_2}{R_1 + R_2} \cdot 12 = \frac{47}{150+47} \cdot 12 = 2,86 \text{ V} ; \quad R_{BB} = R_1 // R_2 = \frac{150 \cdot 47}{150+47} = 35,8 \text{ k}\Omega$$

$$\left. \begin{aligned} I_B &= \frac{V_{BB} - V_{BE} - V_{ce(\infty)}}{R_{BB}} \\ V_{ce(\infty)} &= (1+\beta) I_B \cdot R_4 \end{aligned} \right\} \Rightarrow V_{ce(\infty)} = (1+\beta) \frac{V_{BB} - V_{BE} - V_{ce(\infty)}}{R_{BB}} \cdot R_4$$

$$V_{ce(\infty)} \left(1 + \frac{(1+\beta) R_4}{R_{BB}} \right) = (1+\beta) \frac{R_4}{R_{BB}} (V_{BB} - V_{BE})$$

$$V_{ce(\infty)} \left(1 + 101 \cdot \frac{0,1}{35,8} \right) = 101 \cdot \frac{0,1}{35,8} (2,86 - 0,6)$$

$$\underline{V_{ce(\infty)} = 497 \text{ mV.}}$$

$$V_{ce(t)} = V_{ce(\infty)} \cdot (1 - e^{-\frac{t}{\tau}}) ; \quad \tau = R_{eq} \cdot C_1$$

$$R_{eq} = R_4 // \frac{R_{BB}}{1+\beta} = 0,1 // \frac{35,8}{101} = \frac{0,1 \cdot 0,354}{0,1+0,354} = 78 \text{ }\Omega$$

$$V_{ce(t_0)} = 0,9 \cdot V_{ce(\infty)} = V_{ce(\infty)} \cdot (1 - e^{-\frac{t_0}{\tau}}) \Rightarrow 0,9 = 1 - e^{-\frac{t_0}{\tau}} \Rightarrow 0,1 = e^{-\frac{t_0}{\tau}} ;$$

$$t_0 = \tau \cdot \ln 10 = R_{eq} \cdot C_1 \cdot \ln 10 = 78 \cdot 100 \cdot 10^6 \cdot \ln 10 = \underline{18 \text{ ms.}}$$

(2)

$$0 < V_{BB} < V_{BE} \Rightarrow I_B = 0, \quad I_c = 0 \Rightarrow V_{ce} = 0$$

$$V_{BB(t_1)} = V_{BE} \Rightarrow 10 \cdot \sin \frac{2\pi}{4,1 \cdot 10^3} \cdot t_1 = V_{BE} \Rightarrow t_1 = \frac{4 \cdot 10^3}{2\pi} \arcsin \frac{0,7}{10} = 44,6 \mu\text{s};$$

$$I_{cmax} = \frac{12 - V_{cesat}}{R_2} = \frac{12 - 0,12}{10^3} = 11,8 \text{ mA};$$


$$I_{Bmax} = (V_{BBmax} - V_{BE}) / R_1 = (10 - 0,7) / 10^5 = 93 \mu\text{A}; \quad \beta \cdot I_{Bmax} = \underline{13,95 \text{ mA}}$$


$\beta \cdot I_{Bmax} > I_{cmax}$ (saturation!)

$$\beta I_{Bsat} = 11,8 \text{ mA} \Rightarrow I_{Bsat} = \frac{11,8 \cdot 10^{-3}}{150} = 78,7 \mu\text{A}$$


$$I_{Bsat} = (V_{BBsat} - V_{BE}) / R_1 \Rightarrow V_{BBsat} = R_1 \cdot I_{Bsat} + V_{BE} = 10^5 \cdot 78,7 \cdot 10^{-6} + 0,7 = \underline{8,57 \text{ V}}$$
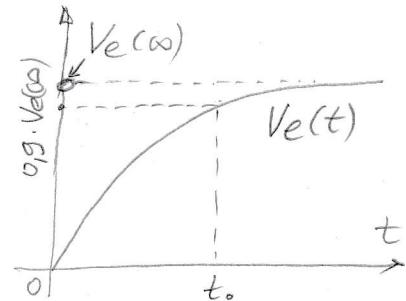
$$V_{BBmax} \cdot \sin \frac{2\pi}{2 \cdot 10^3} t_2 = V_{BBsat} \Rightarrow t_2 = \frac{4 \cdot 10^3}{2\pi} \arcsin \frac{V_{BBsat}}{V_{BBmax}} = \underline{655 \mu\text{s}}$$



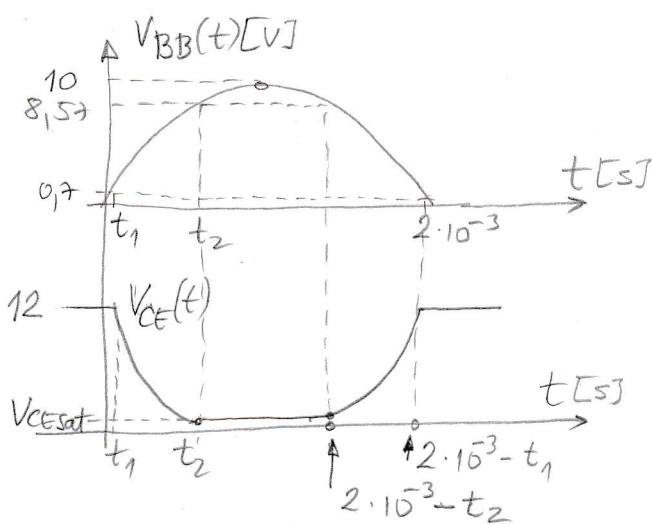
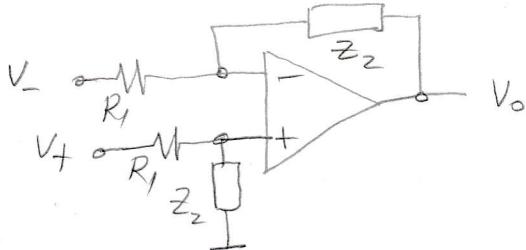
$$\textcircled{3} \quad V_o = -\frac{z_2}{R_1} V_- + \frac{z_2}{R_1 + z_2} \cdot \left(1 + \frac{z_2}{R_1}\right) \cdot V$$



$$\Rightarrow V_o = (V_+ - V_-) \frac{z_2}{R_1}$$

$$z_2 = R_2 \parallel C_2 = \frac{R_2 \cdot \frac{1}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}} = \frac{R_2}{1 + j\omega C_2 R_2}$$

$$V_o = (V_+ - V_-) \frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega C_2 R_2} = (V_+ - V_-) \cdot A_o \frac{1}{1 + j \frac{\omega}{\omega_p}}$$

$$A_o = 10 = \frac{R_2}{R_1} \Rightarrow R_2 = 10 R_1 = \underline{100 \text{ k}\Omega}$$

$$\omega_p = \frac{1}{R_2 C_2} \Rightarrow f_p = \frac{\omega_p}{2\pi} = \frac{1}{2\pi R_2 C_2} = 10^3$$

$$2\pi R_2 C_2 = 10^3 \Rightarrow C_2 = \frac{10^{-3}}{2\pi R_2} = \frac{10^{-3}}{2\pi \cdot 10^5}$$

$$\underline{C_2 = 1,59 \text{ nF}}$$

