
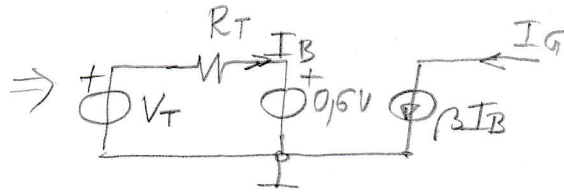


①


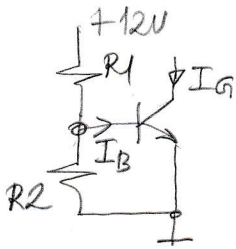


$$V_T = \frac{R_2}{R_1 + R_2} \cdot 12 = 2,863V$$

$$R_T = \frac{R_1 \cdot R_2}{R_1 + R_2} = 35,79k\Omega$$


$$I_B = \frac{V_T - 0,6}{R_T} = \frac{2,863 - 0,6}{35,79 \cdot 10^3} = 63,23 \mu A$$
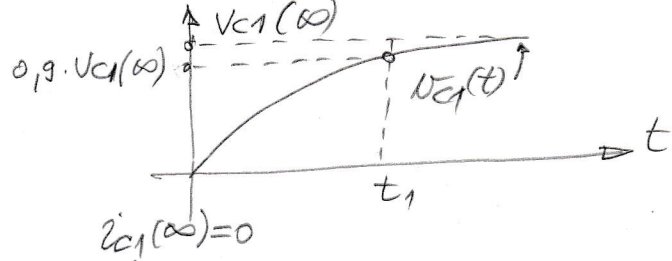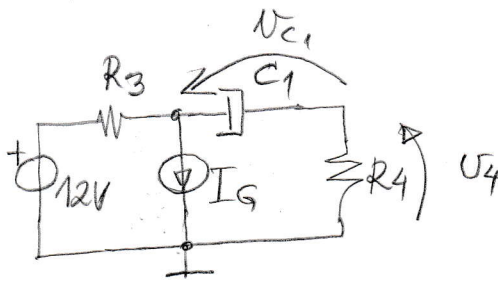
$$I_G = \beta I_B = 100 \cdot 63,23 \cdot 10^{-6} = 6,323 mA$$



$$V_{C1}(0) = 0$$

$$V_{C1}(\infty) = ?$$

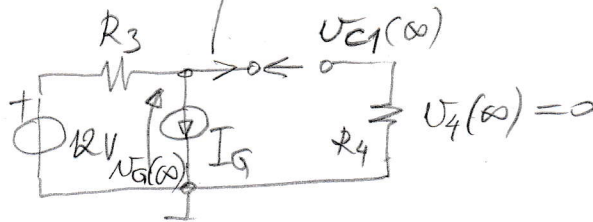

$$V_G(\infty) \cdot \frac{1}{R_3} - 12 \frac{1}{R_3} = -I_G$$

$$V_G(\infty) = 12 - R_3 I_G = 12 - 10^3 \cdot 6,323 \cdot 10^{-3}$$

$$V_G(\infty) = 5,677V \Rightarrow V_{C1}(\infty) = V_G(\infty) - V_4(\infty) = 5,677 - 0 = 5,677V$$

$$V_{C1}(t_1) = 0,9 \cdot V_{C1}(\infty) = V_{C1}(\infty) + [V_{C1}(0) - V_{C1}(\infty)] e^{-\frac{t_1}{\tau}}$$



$$= 5,677 + [0 - 5,677] e^{-\frac{t_1}{\tau}}$$

$$0,1 \cdot 5,677 = 5,677 \cdot e^{-\frac{t_1}{\tau}}$$

$$e^{-\frac{t_1}{\tau}} = 0,1 \Rightarrow e^{+\frac{t_1}{\tau}} = 10 \Rightarrow t_1 = \tau \cdot \ln 10$$

$$\tau = C_1(R_3 + R_4) = 100 \cdot 10^{-6} \cdot 2 \cdot 10^3 = 0,2 ms$$
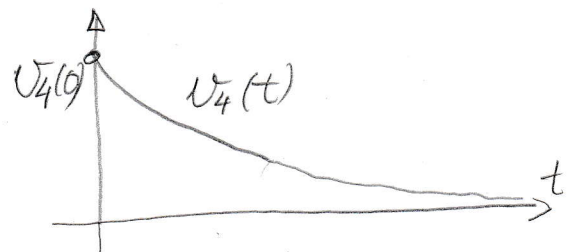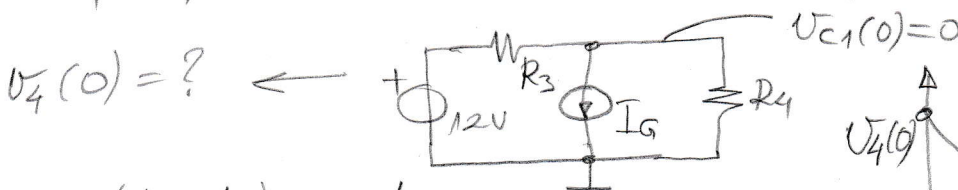
$$t_1 = 0,2 \cdot 10^{-3} \cdot \ln 10 = 0,46 ms = 46 \mu s$$




$$V_4(0) \cdot \left(\frac{1}{R_3} + \frac{1}{R_4}\right) - 12 \cdot \frac{1}{R_3} = -I_G$$

$$V_4(0) = \frac{\frac{12}{R_3} - I_G}{\frac{1}{R_3} + \frac{1}{R_4}} = \frac{\frac{12}{10^3} - 6,323 \cdot 10^{-3}}{\frac{1}{10^3} + \frac{1}{10^3}} = 2,8385V$$

$$V_4(t) = V_4(\infty) + [V_4(0) - V_4(\infty)] \cdot e^{-t/\tau} = V_4(0) \cdot e^{-t/\tau}$$

2

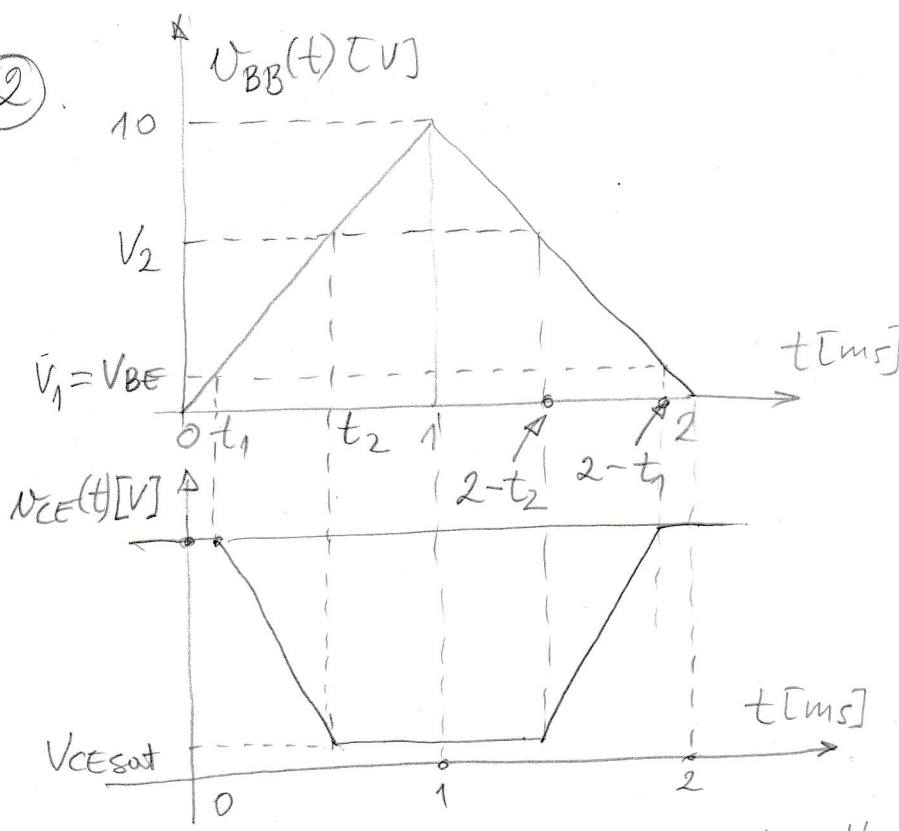

$$V_{BB}(t) = \frac{10}{10^{-3}} t ; 0 < t < 1 \text{ms}$$

$$V_{BB}(t_1) = V_{BE} \Rightarrow \frac{10}{10^3} t = 0,7$$

$$t_1 = \frac{0,7}{10^4} = 70 \mu\text{s}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_1}$$


$$I_{B2} = \frac{V_2 - V_{BE}}{R_1}$$

$$V_{CE} = 12 - R_2 I_C = 12 - R_2 \beta I_B$$

$$V_{CE(sat)} = 12 - R_2 \beta I_{B2} \Rightarrow I_{B2} = \frac{12 - V_{CE(sat)}}{\beta R_2} = \frac{12 - 0,2}{150 \cdot 10^3} = 78,7 \mu\text{A}$$

$$V_2 = V_{BE} + I_{B2} \cdot R_1 = 0,7 + 78,7 \cdot 10^6 \cdot 10^{-5} = 8,57 \text{V} ; V_2 < 10 !$$

3

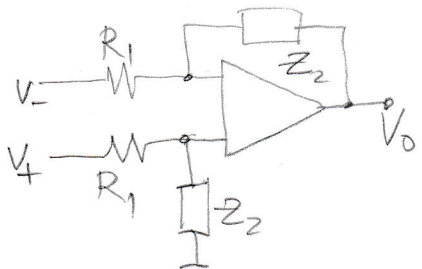

$$V_0 = -V_- \cdot \frac{z_2}{R_1} + \frac{z_2}{R_1 + z_2} \cdot \left(1 + \frac{z_2}{R_1}\right) V_+$$

$$V_0 = (V_+ - V_-) \cdot \frac{z_2}{R_1}$$

$$z_2 = \frac{1}{j\omega C_2}$$

$$A(j\omega) = \frac{V_0}{V_+ - V_-} = \frac{z_2}{R_1} = \frac{1}{j\omega C_2 R_1} = \frac{1}{j \frac{\omega}{\omega_1}} = \frac{1}{j \frac{f}{f_1}}$$

$$\omega_1 = \frac{1}{C_2 R_1} ; f_1 = \frac{1}{2\pi C_2 R_1}$$

$$A(j\omega_1) = 1 \Rightarrow C_2 = \frac{1}{2\pi f R_1} = \frac{1}{2\pi \cdot 10^3 \cdot 10^4} = 15,9 \text{ nF}$$

