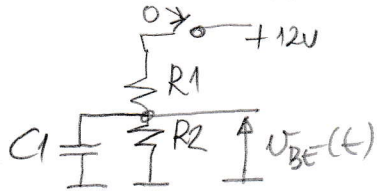


①

$0 < U_{BE} < V_{BE} = 0,6V$



$U_{BE}(0) = 0$

$U_{BE}(\infty) = \frac{R_2}{R_1 + R_2} \cdot 12 = 2,86V$


$\tau = (R_1 || R_2) \cdot C = (47k || 150k) \cdot 10n = \frac{47 \cdot 150}{47 + 150} \cdot 10^{-3} \cdot 10^{-8} = 358\mu s$

$U_{BE}(t) = U_{BE}(\infty) \cdot (1 - e^{-\frac{t}{\tau}})$


$U_{BE}(t_1) = V_{BE}$

$0,6 = 2,86 \cdot (1 - e^{-\frac{t_1}{\tau}}) \Rightarrow \frac{0,6}{2,86} - 1 = -e^{-\frac{t_1}{\tau}} \Rightarrow e^{-\frac{t_1}{\tau}} = 1 - \frac{0,6}{2,86}$

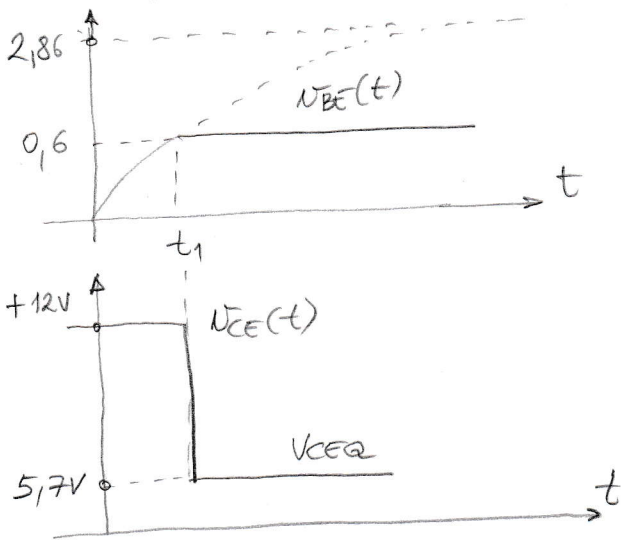$-\frac{t_1}{\tau} = \ln(1 - \frac{0,6}{2,86}) \Rightarrow t_1 = -\tau \cdot \ln(1 - \frac{0,6}{2,86}) = 91\mu s$



$V_T = U_{BE}(\infty) = 2,86V ; R_T = R_1 || R_2 = 35,86k\Omega$

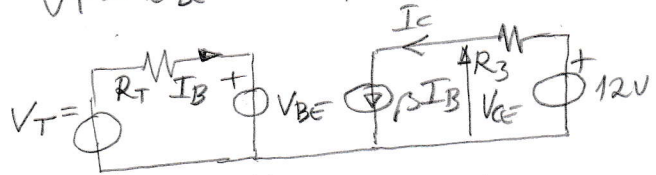

$I_B = \frac{V_T - V_{BE}}{R_T} = 63\mu A$

$I_C = \beta I_B = 100 \cdot 63 \cdot 10^{-6} = 6,3mA$

$V_{CEQ} = 12 - R_3 \cdot I_C = 5,7V$

②

$I_D = \beta (V_{GS} - V_t)^2$

$I_D = 100mA ;$

$V_{GS} = 3,3V$


$\beta = 50 mA/V^2$

$0,1 = 50 \cdot 10^{-3} (3,3 - V_t)^2$


$\frac{0,1}{50 \cdot 10^{-3}} = (3,3 - V_t)^2$

$\sqrt{\frac{0,1}{50 \cdot 10^{-3}}} = 3,3 - V_t$

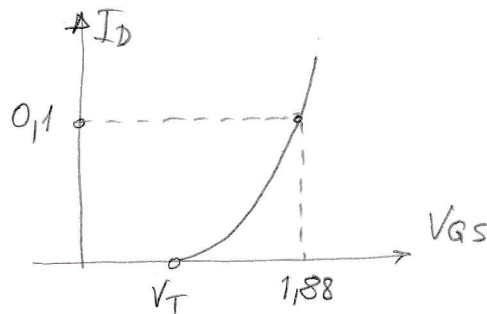$V_t = 3,3 - \sqrt{\frac{0,1}{50 \cdot 10^{-3}}} = 1,88V$




3

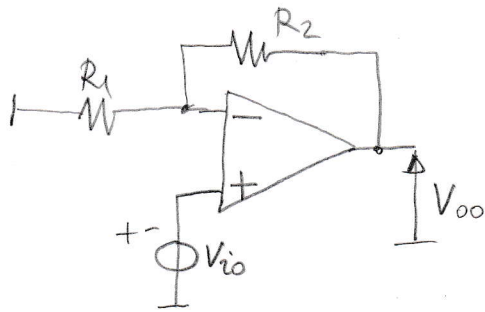

$$V_{oo} = \left(1 + \frac{R_2}{R_1}\right) \cdot V_{io}$$

$$V_{io} = \frac{V_{oo}}{1 + \frac{R_2}{R_1}} = \frac{0,2}{1 + \frac{10^6}{10^4}}$$

$$\underline{V_{io} = 1,98 \text{ mV}}$$

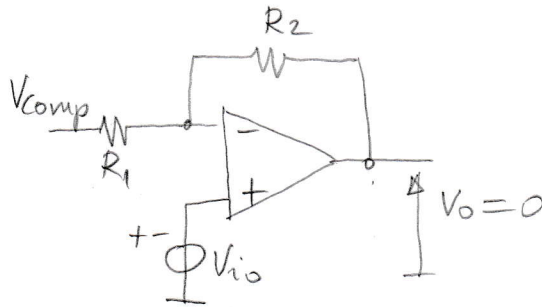

$$V_o = 0 = \underbrace{V_{io} \left(1 + \frac{R_2}{R_1}\right)}_{200 \text{ mV}} - V_{comp} \cdot \frac{R_2}{R_1} = 0$$

$$V_{comp} \cdot \frac{R_2}{R_1} = 0,2$$

$$V_{comp} = \frac{R_1}{R_2} \cdot 0,2 = \frac{10^4}{10^6} \cdot 0,2 = \underline{2 \text{ mV}}$$