
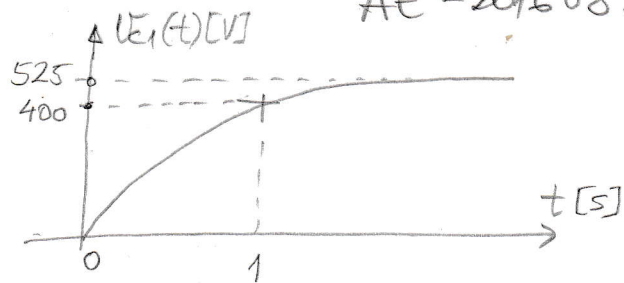


①

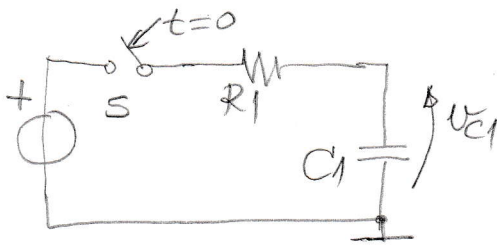

$$U_{C1}(t) = 525 \cdot \left(1 - e^{-\frac{t}{\tau}}\right)$$

$$\tau = R_1 \cdot C_1$$

$$U_{C1}(1) = 400 = 525 \cdot \left(1 - e^{-\frac{1}{\tau}}\right)$$

$$e^{-\frac{1}{\tau}} = 1 - \frac{400}{525} = 0,238 ; e^{\frac{1}{\tau}} = \frac{1}{0,238} = 4,2$$

$$\frac{1}{\tau} = \ln 4,2 ; \tau = \frac{1}{\ln 4,2} = 697 \text{ ms}$$

$$R_1 = \frac{\tau}{C_1} = \frac{697 \cdot 10^{-3}}{10 \cdot 10^{-3}} = \underline{69,7 \Omega}$$

$$W_C = \frac{1}{2} C_1 (U_{C1}(1))^2 = \frac{1}{2} \cdot 10 \cdot 10^{-3} \cdot 400^2 = \underline{800 \text{ J}} = W_R$$

②

$$I_D = \beta (V_{GS} - V_T)^2$$

$$V_{GS} - V_T = \sqrt{\frac{I_D}{\beta}}$$

$$V_T = V_{GS} - \sqrt{\frac{I_D}{\beta}} = 3,3 - \sqrt{\frac{2}{500 \cdot 10^{-3}}} = \underline{1,3 \text{ V}}$$

③

$$V_o = -V_g \frac{R_2}{R_1} \pm (V_{comp} \pm V_{io}) \frac{R_1 + R_2}{R_1}$$

$$V_{o1} = \pm V_{io} \frac{R_1 + R_2}{R_1} = \pm V_{io} \cdot \frac{10^4 + 10^6}{10^4}$$

$$V_{o1} = \pm 101 V_{io}$$

$$V_{io} = \frac{V_{o1}}{101} = \frac{200}{101} = 1,98 \text{ mV}$$

$$V_{comp} \pm V_{io} = 0$$

$$V_{comp} = \pm V_{io} = \underline{\pm 1,98 \text{ mV}}$$