
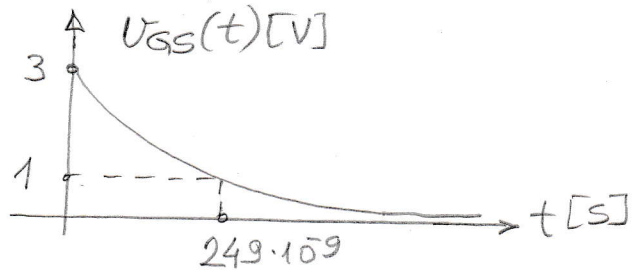


①

$t > 0_+$

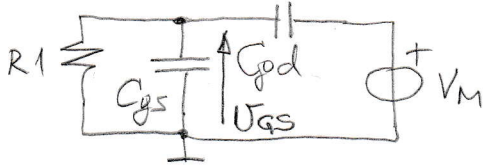

$$U_{GS}(t) = U_{GS}(0) \cdot e^{-\frac{t}{\tau}}$$


$$U_{GS}(0) = \frac{C_{gd}}{C_{gs} + C_{gd}} \cdot V_M = V_T = 3 \text{ V.}$$

$$V_M = V_T \cdot \frac{C_{gs} + C_{gd}}{C_{gd}} = 3 \cdot \frac{1000 + 30}{30} = \underline{103 \text{ V.}}$$

$$\tau = R_1 \cdot (C_{gs} \parallel C_{gd}) = R_1 \cdot (C_{gs} + C_{gd}) = 220 \cdot 1030 \cdot 10^{-12} = \underline{227 \text{ ns}}$$

$$U_{GS}(t_1) = 1 = 3 \cdot e^{-\frac{t_1}{\tau}}; e^{t_1/\tau} = 3; t_1 = \tau \cdot \ln 3 = \underline{249 \text{ ns}}$$

②

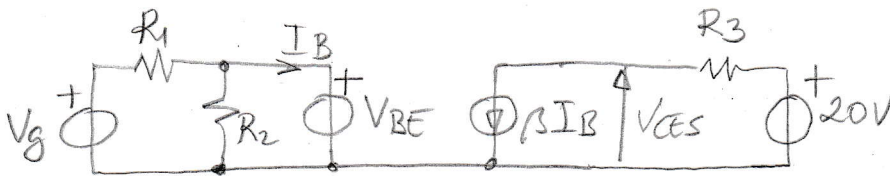

$$I_B = \frac{V_g - V_{BE}}{R_1} - \frac{V_{BE}}{R_2}$$

$$\beta I_B = \frac{20 - V_{CES}}{R_3} = \frac{20 - 0,5}{68} = \underline{287 \text{ mA}}$$

$$I_B = \frac{287 \cdot 10^{-3}}{120} = \underline{2,39 \text{ mA}}$$

$$V_{CES} = 20 - R_3 \cdot \beta I_B$$

$$\frac{V_g - V_{BE}}{R_1} = I_B + \frac{V_{BE}}{R_2} \Rightarrow \frac{V_g}{R_1} = I_B + \frac{V_{BE}}{R_1} + \frac{V_{BE}}{R_2} = 2,39 \cdot 10^{-3} + \frac{0,7}{1000} + \frac{0,7}{470} = \underline{4,58 \text{ mA}}$$

$$V_g = R_1 \cdot 4,58 \cdot 10^{-3} = \underline{4,58 \text{ V}}$$

③

$$V_o = -V_- \cdot A(j\omega)$$

$$V_- (R_2 + R_1) = V_i R_2 + V_o R_1$$

$$V_- = V_i \frac{R_2}{R_1 + R_2} + V_o \frac{R_1}{R_1 + R_2}$$

$$V_- \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - V_i \frac{1}{R_1} - V_o \frac{1}{R_2} = 0$$

$$V_o = - \left[ V_i \frac{R_2}{R_1 + R_2} + V_o \frac{R_1}{R_1 + R_2} \right] \cdot A(j\omega) \Rightarrow A_r(j\omega) = \frac{V_o}{V_i} = - \frac{R_2 A(j\omega)}{R_1 + R_2 + R_1 A(j\omega)}$$

$$A_r = - \frac{R_2 A_o \frac{1}{1 + j\omega/\omega_o}}{R_1 + R_2 + R_1 A_o \frac{1}{1 + j\omega/\omega_o}} = - \frac{R_2 A_o}{(R_1 + R_2)(1 + j\omega/\omega_o) + R_1 A_o}$$

$$A_r = - \frac{R_2 A_o}{R_1 + R_2 + R_1 A_o} \cdot \frac{1}{1 + j \frac{\omega}{\omega_o} \cdot \frac{R_1 + R_2}{R_1 + R_2 + R_1 A_o}} = K \cdot \frac{1}{1 + j \frac{\omega}{\omega_{or}}}$$

$$\omega_{or} = \omega_o \cdot \frac{R_1 + R_2 + R_1 A_o}{R_1 + R_2} = 2\pi \cdot 10 \cdot \frac{10^3 + 10^8 + 10^3 \cdot 10^5}{10^8 + 10^5} \approx 2\pi \cdot 10^4 \text{ rad/s}$$

$$f_r = 10^4 \text{ Hz} = \underline{10 \text{ kHz}}$$