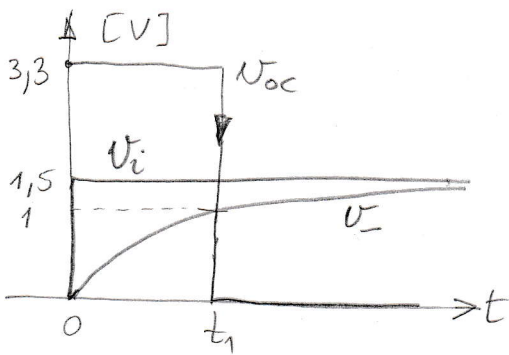


①



$$U_-(t) = V_i \cdot (1 - e^{-\frac{t}{\tau}})$$


$$V_i = 1,5 \text{ V}$$

$$\tau = R_1 \cdot C_1 = 220 \cdot 2,2 \cdot 10^{-9} = \underline{486,2 \text{ ns}}$$

$$U_-(t_1) = 1 = 1,5 \cdot (1 - e^{-\frac{t_1}{\tau}}) \Rightarrow e^{-\frac{t_1}{\tau}} = 1 - \frac{1}{1,5} = \frac{1}{3}$$

$$t_1 = \tau \cdot \ln 3 = \underline{534 \text{ ns}}$$

②

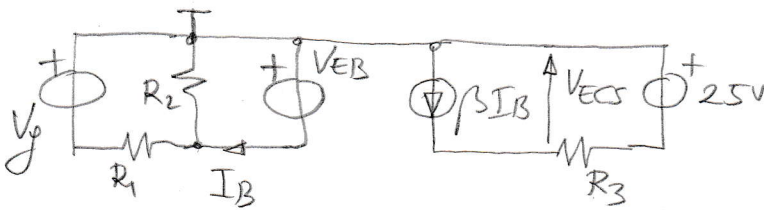

$$I_B = \frac{V_g - V_{EB}}{R_1} - \frac{V_{EB}}{R_2} \quad \beta I_B = \frac{25 - V_{ECS}}{R_3} = \frac{25 - 0,6}{47} = \underline{519 \text{ mA}}$$

$$V_{ECS} = 25 - R_3 \beta I_B \quad I_B = \frac{519}{100} \cdot 10^3 = \underline{5,19 \text{ mA}}$$

$$\frac{V_g - V_{EB}}{R_1} = I_B + \frac{V_{EB}}{R_2} \Rightarrow \frac{V_g}{R_1} = I_B + \frac{V_{EB}}{R_2} + \frac{V_{EB}}{R_1} = 5,19 \cdot 10^{-3} + \frac{0,8}{330} + \frac{0,8}{680}$$

$$\frac{V_g}{R_1} = 8,79 \text{ mA}; \quad V_g = R_1 \cdot 8,79 \text{ mA} = 680 \cdot 8,79 \cdot 10^{-3} = \underline{5,98 \text{ V}}$$

③

$$\left. \begin{aligned} V_o &= (V_i - V_-) \cdot A(j\omega) \\ V_- &= V_o \cdot \frac{R_1}{R_1 + R_2} \end{aligned} \right\} \rightarrow V_o = V_i \cdot A(j\omega) - V_o \frac{R_1}{R_1 + R_2} \cdot A(j\omega)$$

$$A_r(j\omega) = \frac{V_o}{V_i} = \frac{A(j\omega)}{1 + \frac{R_1}{R_1 + R_2} A(j\omega)}$$

$$A_r(j\omega) = \frac{A_0 \frac{1}{1 + j\omega/\omega_0}}{1 + \frac{R_1}{R_1 + R_2} \cdot A_0 \frac{1}{1 + j\omega/\omega_0}} = \frac{A_0}{1 + j\omega/\omega_0 + \frac{A_0 R_1}{R_1 + R_2}}$$

$$A_r(j\omega) = \frac{A_0}{1 + \frac{A_0 R_1}{R_1 + R_2}} \cdot \frac{1}{1 + j \frac{\omega}{\omega_0 \cdot \frac{A_0 R_1}{R_1 + R_2}}} = K \cdot \frac{1}{1 + j \frac{\omega}{\omega_r}}$$

$\omega_r = \omega_0 \cdot \frac{A_0 R_1}{R_1 + R_2}$

$$\omega_r = \omega_0 \cdot \frac{A_0 R_1}{R_1 + R_2} = 2\pi \cdot 10 \cdot \frac{10^5 \cdot 10^3}{10^3 + 10^5} \approx 2\pi \cdot 10^4 \text{ rad/s}$$

$$f_r = \frac{\omega_r}{2\pi} = 10^4 \text{ Hz} = \underline{10 \text{ kHz}}$$