
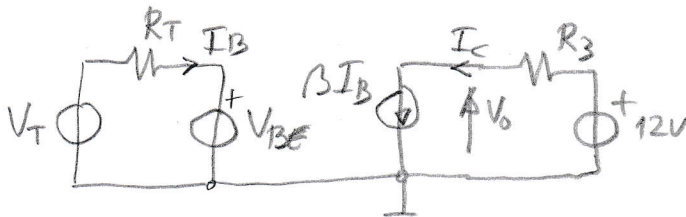


1

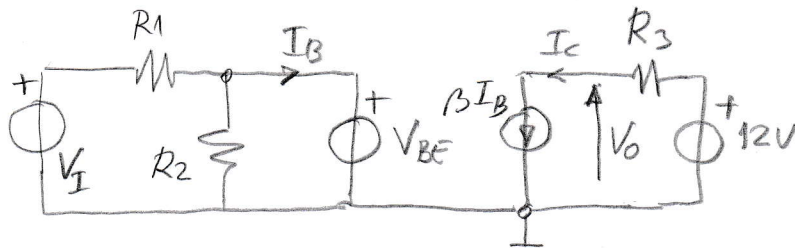

$$V_T = \frac{R_2}{R_1 + R_2} \cdot V_I = 0,244 V_I$$

$$R_T = R_1 || R_2 = 22 || 68 = 16,62 k\Omega$$

$$V_T < V_{BE} \Rightarrow I_B = 0 ; I_C = 0 ; V_o = 12 - R_3 I_C = 12V$$

$$V_T = \frac{R_2}{R_1 + R_2} V_I < 0,7 \Rightarrow V_I < 0,7 \cdot \frac{R_1 + R_2}{R_2} = 0,7 \cdot \frac{90}{22} = 2,86V$$

$$V_I > 2,86V :$$

$$I_B = \frac{V_T - V_{BE}}{R_T} = V_I \cdot \frac{R_2}{R_1 + R_2} \cdot \frac{R_1 + R_2}{R_2 R_1} - V_{BE} \cdot \frac{R_1 + R_2}{R_1 \cdot R_2} = \frac{V_I}{R_1} - \frac{0,7}{16,62k} = \frac{V_I}{68k} - 42 \mu$$

$$V_I = 0 \Rightarrow V_o = 12V ; V_I = 1V \Rightarrow V_o = 12V ; V_I = 2V \Rightarrow V_o = 12V ;$$

$$V_I = 3V \Rightarrow I_B = 2,12 \mu A \Rightarrow V_o = 12 - 150 \cdot 2,12 \cdot 10^{-6} \cdot 10^3 = 11,68V$$

$$V_I = 4V \Rightarrow I_B = 16,8 \mu A \Rightarrow V_o = 9,48V ;$$

$$V_I = 5V \Rightarrow I_B = 31,53 \mu A \Rightarrow V_o = 7,2V ;$$

$$V_I = 6V \Rightarrow I_B = 46,24 \mu A \Rightarrow V_o = 5,06V ;$$

$$V_I = 7V \Rightarrow I_B = 60,94 \mu A \Rightarrow V_o = 2,86V ;$$

$$V_I = 8V \Rightarrow I_B = 75,65 \mu A \Rightarrow V_o = 0,65V ;$$

$$V_I = 9V \Rightarrow I_B = 90,35 \mu A \Rightarrow V_o = -1,55V ! \Rightarrow V_o = V_{CEsat} = 0,2V$$

$$V_I = 10, 11, 12V \Rightarrow V_o = 0,2V$$

