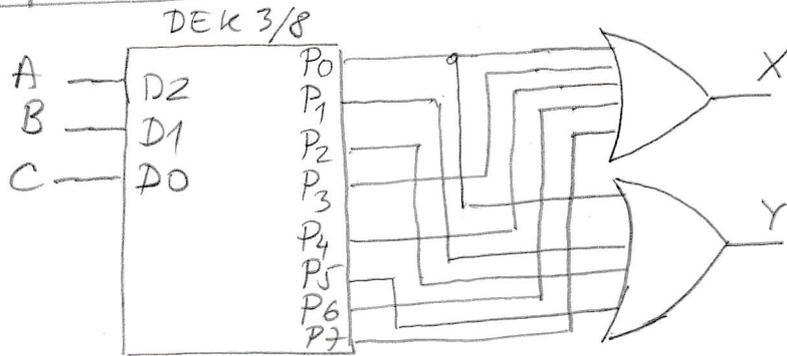


1

n	A	B	C	X	Y
0	0	0	0	1	1
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	1	0
7	1	1	1	1	0






$$X = P_0 + P_3 + P_4 + P_6 + P_7$$

$$Y = P_0 + P_1 + P_2 + P_5$$




2

n	Qn				Qn+1			
	D	C	B	A	D	C	B	A
0	0	0	0	0	0	0	0	1
1	0	0	0	1	0	0	1	1
3	0	0	1	0	0	1	1	0
2	0	0	1	1	0	0	1	0
7	0	1	0	0	1	1	0	0
6	0	1	0	1	0	1	0	0
4	0	1	1	0	0	1	1	1
5	0	1	1	1	0	1	0	1
-	1	0	0	0	X	X	X	X
-	1	0	0	1	X	X	X	X
-	1	0	1	0	X	X	X	X
-	1	0	1	1	X	X	X	X
8	1	1	0	0	1	1	0	1
9	1	1	0	1	0	0	0	0
-	1	1	1	0	X	X	X	X
-	1	1	1	1	X	X	X	X

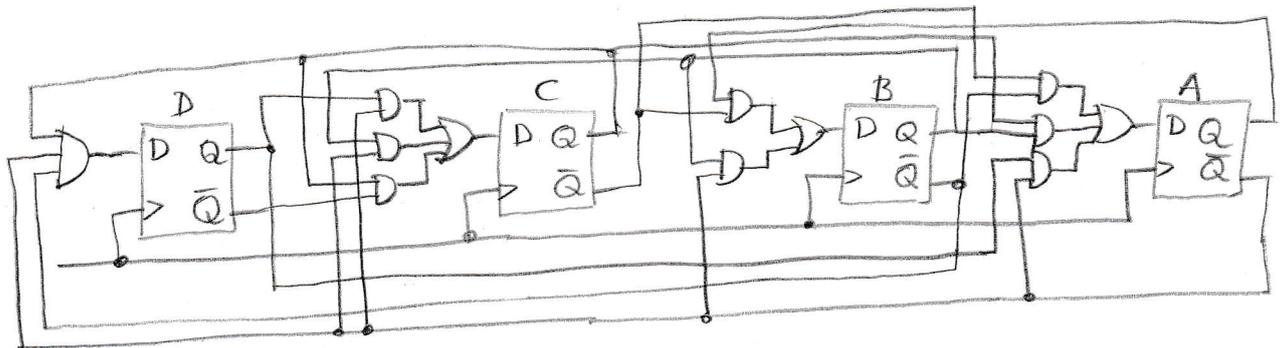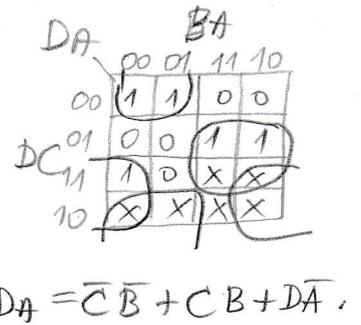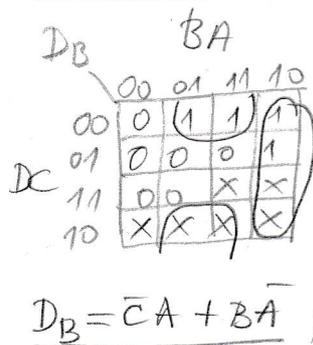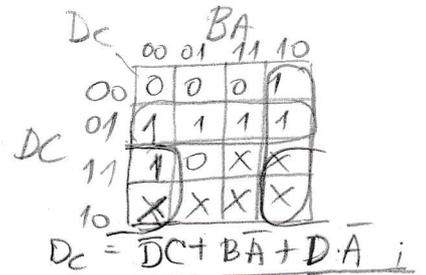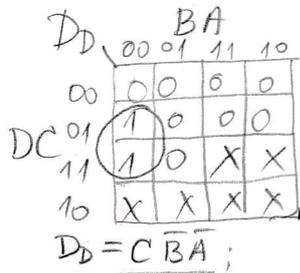

3

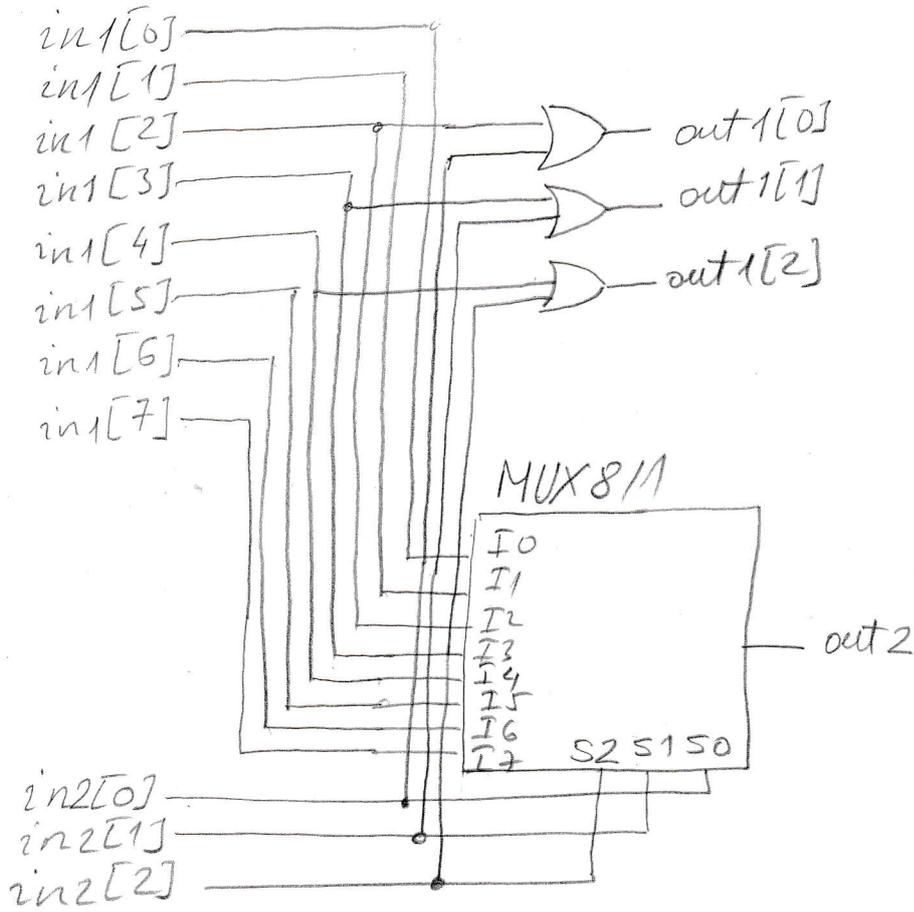

4

