

$$① \quad V_o = \overline{|V_s|} - 2 \cdot 1,5 - 1 \text{ [V]}$$

$$V_{seff} = \frac{N_s}{N_p} \cdot 400 \leftarrow V_{peff}$$

$$\overline{|V_s|} = \frac{1}{T/2} \int_0^{T/2} V_s(t) dt = \frac{2}{T} \int_0^{T/2} V_{sm} \sin \omega t dt = \frac{V_{seff} \cdot \sqrt{2} \cdot 2}{\pi}$$

$$V_o = \frac{V_{seff} \sqrt{2} \cdot 2}{\pi} - 4; \quad V_{seff} = (V_o + 4) \frac{\pi}{2\sqrt{2}};$$

$$V_{seffmin} = (V_{o,max} + 4) \frac{\pi}{2\sqrt{2}} = (9 + 4) \cdot \frac{\pi}{2\sqrt{2}} = 14,44 \text{ V}$$

$$N_{smin} = V_{seffmin} \cdot \frac{N_p}{400} = 14,44 \cdot \frac{150}{400} = 5,4 \approx 6$$

$$② \quad D = \frac{V_{out}}{V_{in}} = \frac{15}{50} = 0,3 = 30\%.$$

$$\Delta I_L = \frac{V_{out} \cdot D}{f \cdot L} \Rightarrow L = \frac{V_{out} \cdot (1-D)}{f \cdot \Delta I_L} = \frac{15 \cdot 0,7}{70 \cdot 10^3 \cdot 10} = 15 \mu\text{H}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}} \Rightarrow C = \frac{1}{4\pi^2 f_r^2 \cdot L} = \frac{1}{4\pi^2 \cdot (1,5 \cdot 10^3)^2 \cdot 15 \cdot 10^{-6}} = 750 \mu\text{F}$$

$$③ \quad P_D = (1-D) V_D \cdot I_o$$

$$P_D = 0,7 \cdot 0,8 \cdot 20 = 11,2 \text{ W}$$

$$P_Q = \frac{1}{T} \int_0^{DT} \left(15 + \frac{10}{DT} t\right)^2 R_{DSon} dt$$

$$P_Q = \frac{1}{T} \int_0^{DT} \left(15^2 + \frac{300}{DT} t + \frac{100}{D^2 T^2} t^2\right) R_{DSon} \cdot dt.$$

$$P_Q = \frac{R_{DSon}}{T} \left[15^2 \cdot DT + \frac{300}{DT} \cdot \frac{(DT)^2}{2} + \frac{100}{D^2 T^2} \cdot \frac{(DT)^3}{3} \right]$$

$$P_Q = 70 \cdot 10^{-3} \cdot 6 \cdot 10^{-3} \left[15^2 \cdot 0,3 \frac{1}{70 \cdot 10^3} + \frac{300 \cdot 0,3}{2 \cdot 70 \cdot 10^3} + \frac{100}{3} \cdot \frac{0,3}{70 \cdot 10^3} \right]$$

$$P_Q = 420 [964 \cdot 10^{-6} + 643 \cdot 10^{-6} + 143 \cdot 10^{-6}]$$

$$P_Q = 0,735 \text{ W}$$

