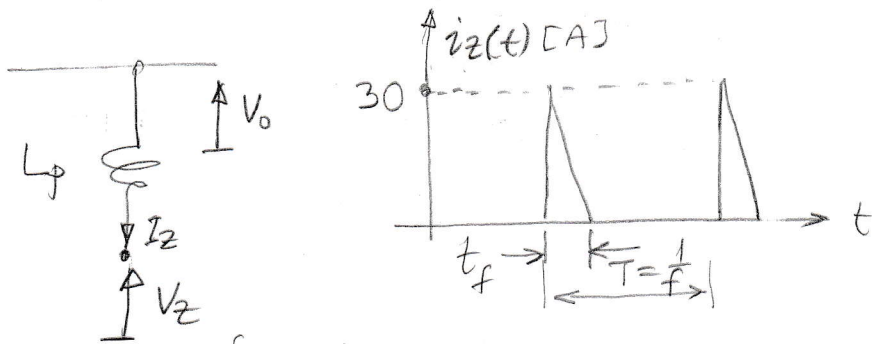


①



$$I_{Qmax} = \frac{\int_{t_f} v_p dt}{L_p} = \frac{(V_2 - V_0) \cdot t_f}{L_p} \Rightarrow t_f = \frac{I_{Qmax} \cdot L_p}{V_2 - V_0}$$

$$t_f = \frac{30 \cdot 500 \cdot 10^{-9}}{100 - 50} = 300 \text{ ns};$$


$$P_{2max} = I_{Qmax} \cdot V_2 = 30 \cdot 100 = 3 \text{ kW};$$

$$\overline{P}_2 = W_2 \cdot f_s; \quad W_2 = \int_0^{t_f} i_2(t) \cdot v_2(t) dt = \int_0^{t_f} i_2(t) \cdot 100 dt$$

$$W_2 = 100 \cdot t_f \cdot \frac{I_{Qmax}}{2} = 100 \cdot 300 \cdot 10^{-9} \cdot \frac{30}{2} = 450 \mu\text{J}.$$

$$\overline{P}_2 = 450 \cdot 10^6 \cdot 30 \cdot 10^{-3} = 13,5 \text{ W}.$$

②

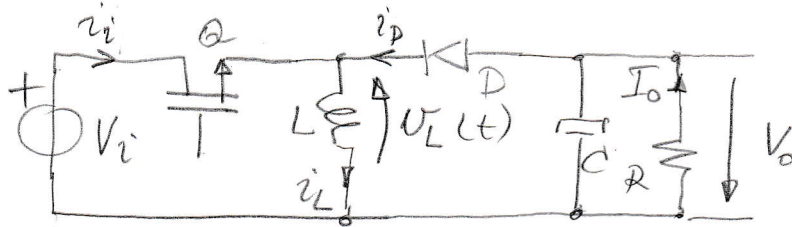

$$a) V_i D T = (V_{oa} + V_D)(1-D)T;$$

$$12 \cdot 0,5 = (V_{oa} + 1) \cdot 0,5;$$

$$12 = V_{oa} + 1 \Rightarrow V_{oa} = 11 \text{ V}.$$

$$b) (V_i - I_i r_{Dson}) D T = (V_{ob} + V_D)(1-D)T$$

$$i_i(t) = i_L(t) \quad 0 < t < DT;$$

$$i_D(t) = i_L(t) \quad DT < t < T;$$


$$I_o = \overline{i_D(t)} = I_L \cdot (1-D) \Rightarrow I_L = \frac{I_o}{1-D} = \frac{I_o}{1-0,5} = 2I_o$$

$$(V_i - I_L r_{Dson}) D T = (V_{ob} + V_D)(1-D)T$$

$$V_{ob} = V_{oa} \cdot 0,97 = 11 \cdot 0,97 = 10,67;$$


$$r_{Dson} = \frac{V_i + V_{ob} + V_D}{I_L} = \frac{V_i + V_{ob} + V_D}{2I_o} = \frac{12 - 10,67 - 1}{50}$$
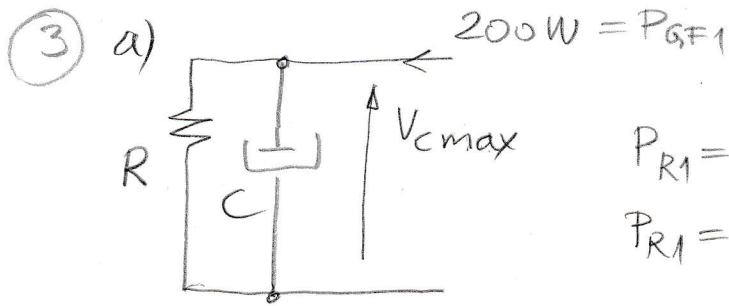
$$r_{Dson} = \frac{0,33}{50} = 6,6 \text{ m}\Omega$$



$$P_{R1} = P_{GF1}$$
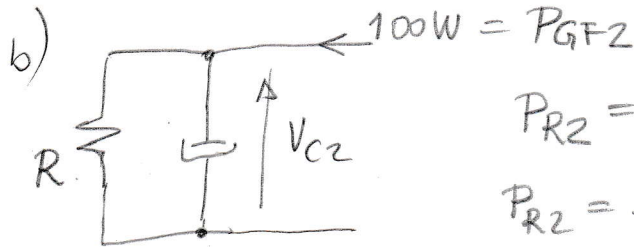
$$P_{R1} = \frac{V_{Cmax}^2}{R} \Rightarrow R = \frac{V_{Cmax}^2}{P_{R1}} = \underline{1250 \Omega}$$



$$P_{R2} = P_{GF2}$$

$$P_{R2} = \frac{V_{C2}^2}{R} \Rightarrow V_{C2} = \sqrt{P_{R2} \cdot R} = \underline{353 V}$$

$$V_{C2} < 230 \cdot \sqrt{2} !$$
