
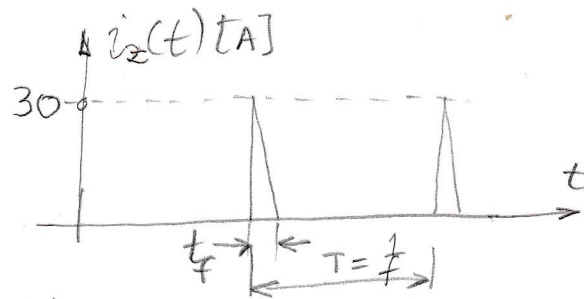


①

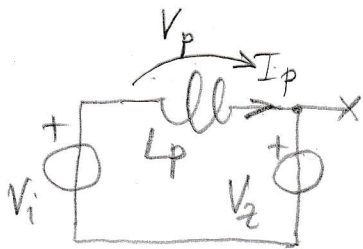

$$I_{Qmax} = \frac{\int_{t_f} V_p(t) dt}{L_p} = \frac{(V_z - V_i) t_f}{L_p} \Rightarrow t_f = \frac{I_{Qmax} \cdot L_p}{V_z - V_i}$$

$$t_f = \frac{30 \cdot 500 \cdot 10^{-9}}{100 - 48} = 288 \text{ ns}$$


$$P_{zmax} = I_{Qmax} \cdot V_z = 30 \cdot 100 = 3 \text{ kW};$$

$$\bar{P}_z = W_z \cdot f_s; \quad W_z = \int_0^{t_f} i_z(t) \cdot v_z(t) dt = \int_0^{t_f} i_z(t) \cdot 100 dt$$

$$W_z = 100 \cdot t_f \cdot \frac{I_{Qmax}}{2} = 100 \cdot 288 \cdot 10^{-9} \cdot \frac{30}{2} = 432 \mu\text{J}$$

$$\bar{P}_z = 432 \cdot 10^{-6} \cdot 30 \cdot 10^3 = 12,96 \text{ W}$$

②

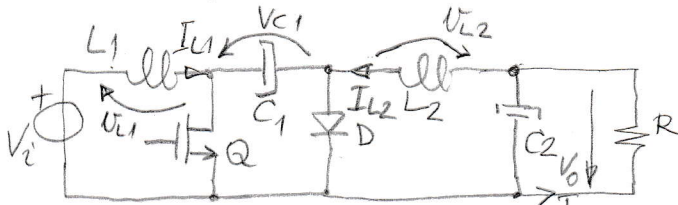

$$a) \quad V_i D T = (V_{c1a} + V_D - V_i)(1-D)T \Rightarrow V_i D = V_{c1a} + V_D - V_i - V_{c1a} D - V_D D + V_i D$$

$$-V_{c1a}(1-D) = V_D(1-D) - V_i$$

$$V_{c1a} = \frac{V_i}{1-D} - V_D = \frac{12}{0,5} - 1 = 23 \text{ V}$$

$$(V_{c1a} - V_{o1}) D T = (V_{o1} + V_D)(1-D)T$$

$$V_{c1a} D - V_{o1} D = V_{o1} + V_D - V_{o1} D - V_D D$$

$$V_{c1a} = \frac{V_{o1} + (1-D)V_D}{D} = \frac{V_{o1} + 0,5 \cdot 1}{0,5}$$

$$= 2V_{o1} + 1$$

$$23 = 2V_{o1} + 1 \Rightarrow V_{o1} = \frac{22}{2} = 11 \text{ V}$$

$$b) \quad [V_i - (I_{L1} + I_{L2}) r_{DSon}] D T = (V_{c1b} + V_D - V_i)(1-D)T$$

$$V_i D - (I_{L1} + I_{L2}) r_{DSon} D = V_{c1b} + V_D - V_i - V_{c1b} D - V_D D + V_i D$$

$$V_{c1b} = \frac{V_i - (1-D)V_D - (I_{L1} + I_{L2}) \cdot r_{DSon}}{1-D}$$

$$(V_{c1b} - V_{o2} - (I_{L1} + I_{L2}) r_{DSon}) D T = (V_{o2} + V_D)(1-D)T$$

$$V_{c1b} D - V_{o2} D - (I_{L1} + I_{L2}) \cdot r_{DSon} D = V_{o2} + V_D - V_{o2} D - V_D D$$

$$V_{C1b} = \frac{V_{ob} + V_D(1-D) + r_{DSon}(I_{L1} + I_{L2}) \cdot D}{D}$$


$$I_{L2} = I_o = 25 \text{ A.}$$

$$D I_{L2} = (1-D) I_{L1} \Rightarrow I_{L1} = \frac{D I_{L2}}{1-D} = \underline{25 \text{ A}} ; V_{ob} = 0,97 \cdot V_{oa} = \underline{10,67 \text{ V}}$$

$$\frac{V_i - (1-D)V_D - (I_{L1} + I_{L2}) \cdot r_{DSon}}{1-D} = \frac{V_{ob} + (1-D)V_D + (I_{L1} + I_{L2}) r_{DSon} \cdot D}{D}$$

$$\frac{12 - 0,5 \cdot 1 - 50 \cdot r_{DSon}}{0,5} = \frac{V_{ob} + 0,5 \cdot 1 + 50 \cdot r_{DSon} \cdot 0,5}{0,5}$$
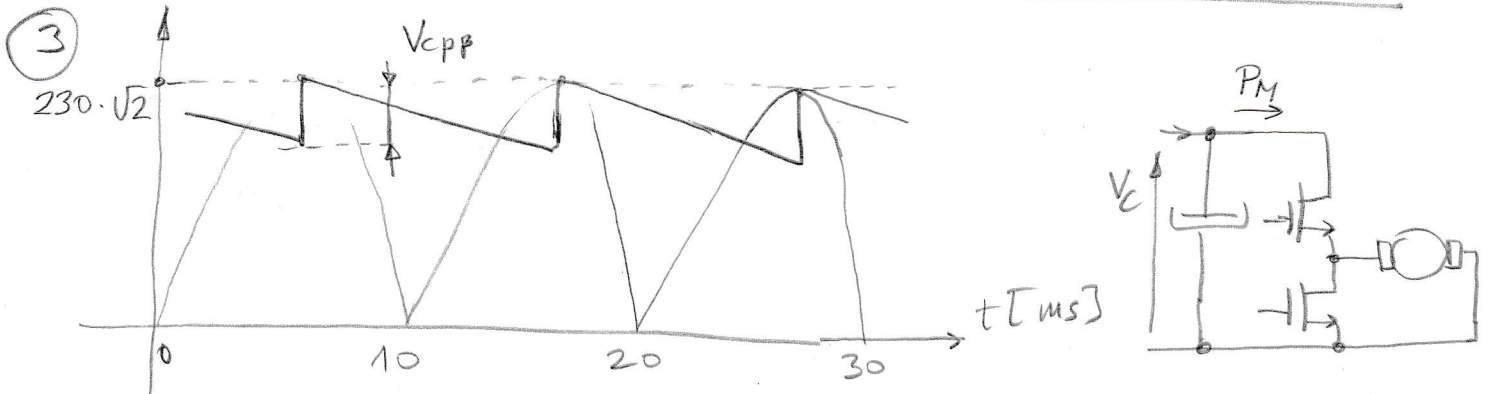
$$12 - 0,5 - 0,5 - 75 r_{DSon} = V_{ob} \Rightarrow r_{DSon} = \frac{11 - V_{ob}}{75} = \frac{0,33}{75} = \underline{4,4 \text{ m}\Omega}$$



$$P_M = V_M \cdot I_M = 120 \cdot 15 = \underline{1800 \text{ W}}$$

$$W_M = P_M \cdot \frac{T}{2} = 1800 \cdot 10 \cdot 10^{-3} = \underline{18 \text{ J}}$$

$$W_M = \frac{1}{2} C (V_{C_{\max}}^2 - V_{C_{\min}}^2)$$

$$C = \frac{2 W_M}{V_{C_{\max}}^2 - V_{C_{\min}}^2} = \frac{36}{(230\sqrt{2})^2 - (230\sqrt{2} - 50)^2} = \underline{1,2 \text{ mF}}$$