


1

$$p(t) = 500 \cdot \sin \left[\frac{2\pi}{24}(t-6) \right]$$

$$p_o(t) = 0,9 \cdot 500 \cdot \sin \left[\frac{2\pi}{24}(t-6) \right] = 450 \cdot \sin \left[\frac{2\pi}{24}(t-6) \right]$$

$$W_o = \int_6^{18} p_o(t) dt = \frac{2}{\pi} 12 \cdot 450 = \underline{3,44 \text{ [kWh]}}$$
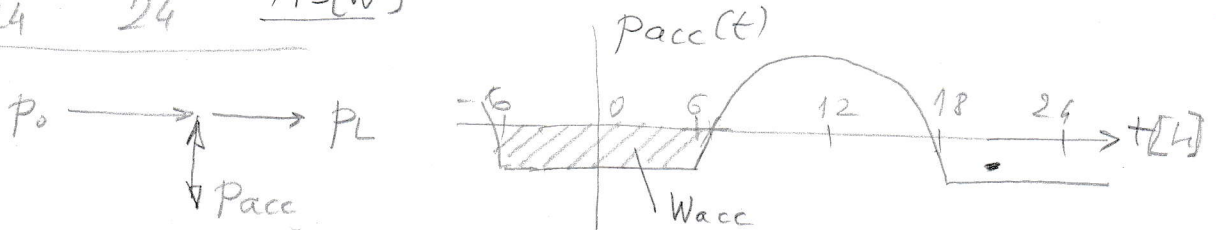
$$P_L = \frac{W_o}{24} = \frac{3440}{24} = \underline{143 \text{ [W]}}$$




$$W_{acc} \approx 12 \cdot 143 = \underline{1,72 \text{ [kWh]}}$$

$$Q = \frac{W_{acc}}{U} = \frac{1716}{24} = \underline{71,5 \text{ [Ah]}}$$

2
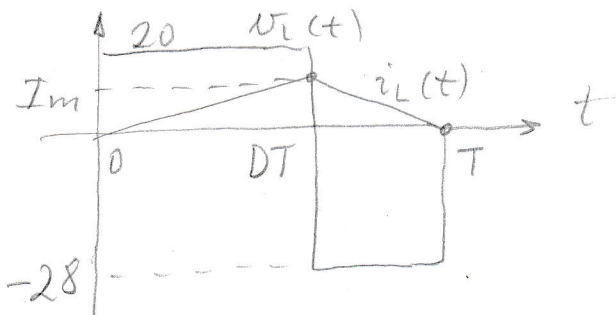
$$U_B = \frac{D}{1-D} V_p \Rightarrow U_B(1-D) = D \cdot V_p \Rightarrow 28(1-D) = 20D; D = \underline{58,3\%}$$




$$I_p = I_m D / 2 \Rightarrow I_m = \frac{2}{D} I_p = \frac{2}{0,583} \cdot 7 = \underline{24 \text{ [A]}}$$

$$v_L(t) = L \frac{di_L}{dt} \Rightarrow L = \frac{v_L}{di/dt}$$

$$L = \frac{20}{24 / (0,583 \cdot 20 \mu s)} = \underline{9,7 \text{ [μH]}}$$

3

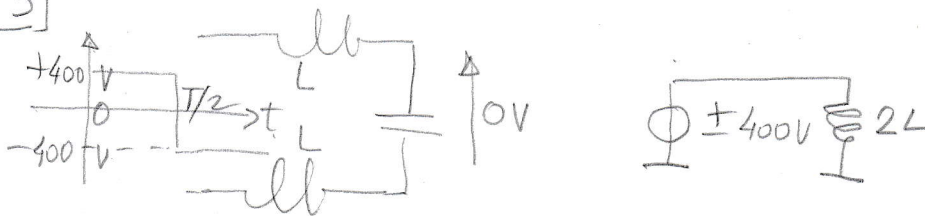

$$\Delta I_L = \frac{V_m \cdot \frac{1}{2} T}{2L} = \frac{\pm 400}{4fL} \Rightarrow L = \frac{400}{4f \Delta I_L} = \frac{400}{4 \cdot 20 \cdot 10^3 \cdot 1} = \underline{5 \text{ [mH]}}$$