

① a) $U_a = 25V, I_a = 20A \quad P_a = 25 \cdot 20 = 500W$

b) $U_b = 25 + \Delta U; I_b = 20 - \Delta I$

$U_b = 25 + \Delta U; I_b = 20 - \Delta U \cdot \frac{20}{5}; \quad P_b \approx 25 \cdot 20 + \Delta U \cdot 20 - 25 \cdot \Delta U \cdot \frac{20}{5} = 500 - \Delta U \cdot 100$

$P_b < P_a = 500W$

c) $U_c = 25 - \Delta U; I_c = 20 + \Delta I$


$U_c = 25 - \Delta U; I_c = 20 + \frac{5}{25} \cdot \Delta U; \quad P_c \approx 25 \cdot 20 - 20 \Delta U + 25 \cdot \frac{5}{25} \Delta U = 500 - 15 \Delta U$

$P_c < P_a = 500W$

$P_{max} = P_a = 500W; \quad U_a = 25V, I_a = 20A.$

② $V_o = V_I \cdot \frac{N_s}{N_p} \cdot D; \quad V_{omin} = 200 \cdot \frac{1}{10} \cdot 0,45 = 9V$

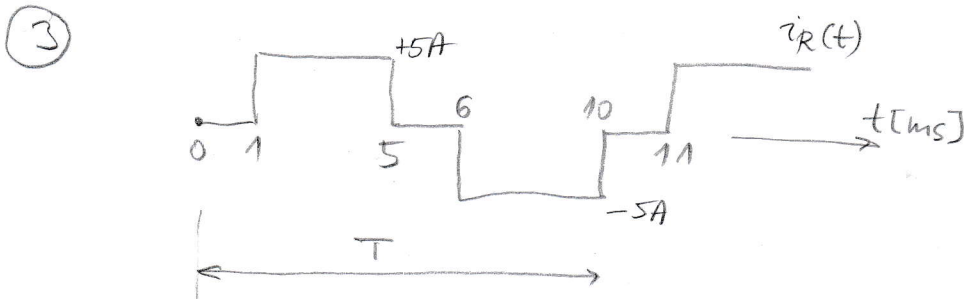$n = \frac{V_{omin}}{V_m} = \frac{9}{4,2} = 2,14 \times 2$



$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i_R^2(t) dt}$

$= \sqrt{\frac{1}{10ms} \cdot 5^2 \cdot 8ms} = 5 \sqrt{\frac{8}{10}} = 4,47 [A]$