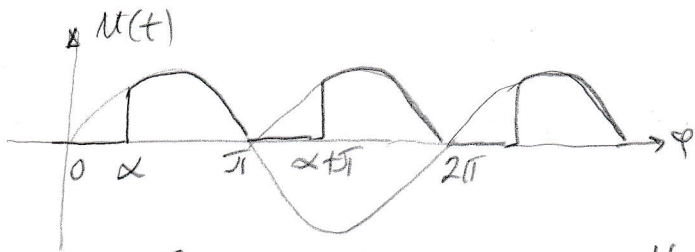


①



$$u_M(t) = \begin{cases} 0 & 0 < \varphi < \alpha \\ U_m \sin \varphi, & \alpha < \varphi < \pi \end{cases}$$

$$U_M = \frac{1}{\pi} \int_{\alpha}^{\pi} U_m \sin \varphi d\varphi$$

$$U_M = \frac{230\sqrt{2}}{\pi} (-\cos \varphi) \Big|_{\alpha}^{\pi} = \frac{230\sqrt{2}}{\pi} (1 + \cos \alpha)$$

$$U_{M1} = 50V \Rightarrow 50\pi = (1 + \cos \alpha) 230\sqrt{2}$$

$$\cos \alpha_1 = \frac{50\pi}{230\sqrt{2}} - 1 \Rightarrow \alpha_1 = \arccos\left(\frac{50\pi}{230\sqrt{2}} - 1\right) = 121^\circ$$


$$U_{M2} = 150V \Rightarrow \cos \alpha_2 = \frac{150\pi}{230\sqrt{2}} - 1 \Rightarrow \alpha_2 = \arccos\left(\frac{150\pi}{230\sqrt{2}} - 1\right) = 63^\circ$$

$$\textcircled{2} \quad P_{I\max} = 48V \cdot 10A = 480W$$


$$P_{0\max} = P_{I\max} = V_0 \cdot I_{0\max} \Rightarrow I_{0\max} = \frac{P_{0\max}}{V_0}$$

$$I_{0\max 1} = \frac{P_{0\max}}{V_{01}} = \frac{480W}{12V} = 40A$$
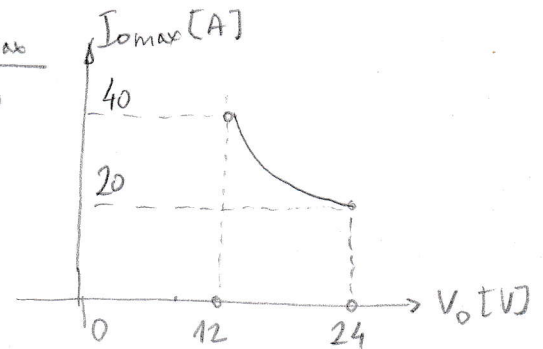
$$I_{0\max 2} = \frac{P_{0\max}}{V_{02}} = \frac{480W}{24V} = 20A$$



③

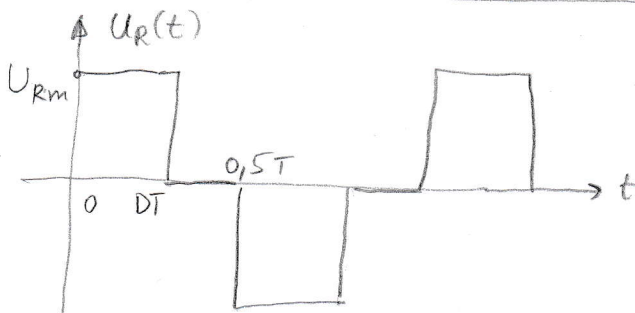

$$U_{Rm} = 24 \cdot 12 = 288V$$

$$P_R = \frac{1}{R} \frac{1}{T} \int_0^T u_R^2(t) dt = \frac{1}{R} \frac{2}{T} \int_0^{DT} 288^2 dt = \frac{2 \cdot 288^2}{RT} \cdot DT$$

$$P_R = D \cdot \frac{2 \cdot 288^2}{100} \Rightarrow D = \frac{P_R}{\frac{2 \cdot 288^2}{100}} = \frac{400 \cdot 100}{2 \cdot 288^2} = 0,241$$